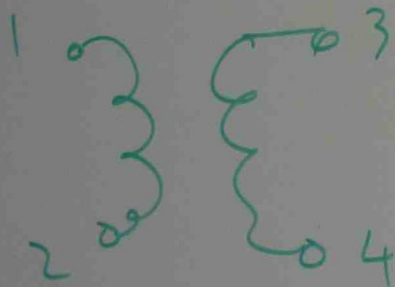



# SOLVING SIMULTANEOUS EQUATIONS IN POWER ENGINEERING PROBLEMS

MATHEMATICAL MODELLING - REPRESENTING ELECTRICAL MODEL BY  
MATHEMATICAL EQUATIONS.


## MATHEMATICAL EQUATIONS FOR FOUR TERMINAL NETWORKS




TRANSFORMER

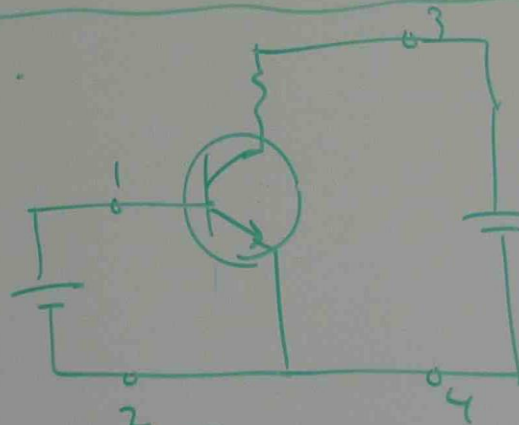

TRANSISTOR

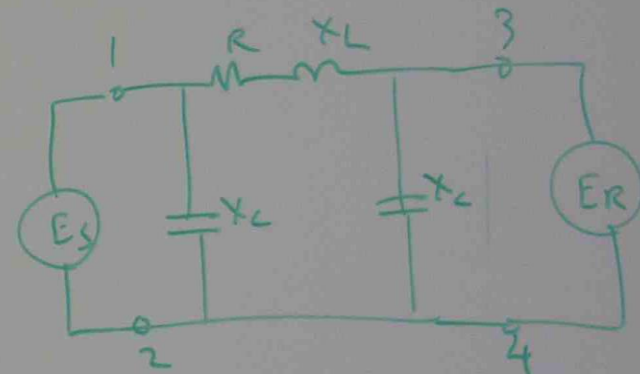


TRANSMISSION LINE

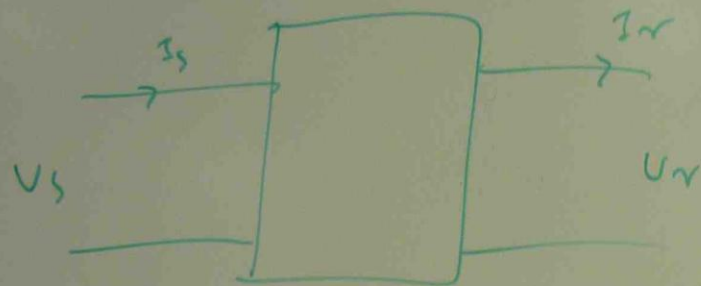

$$\overline{V}_s = A \overline{V}_r + B \overline{I}_r$$
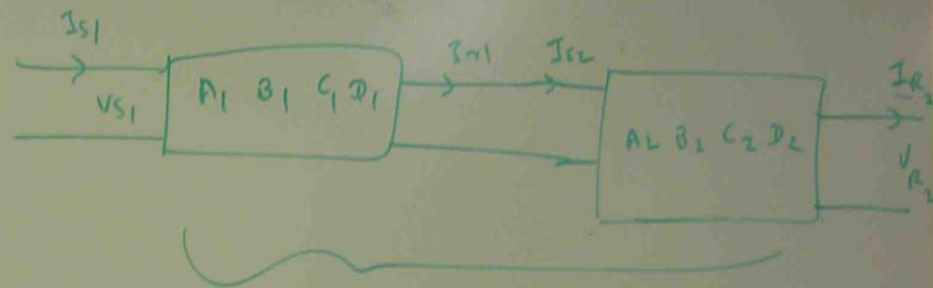
$$\overline{I}_s = C \overline{V}_r + D \overline{I}_r$$



$$A_{eq} = A_1 A_2 + B_1 C_2$$

$$B_{eq} = A_1 B_2 + B_1 D_2$$

$$C_{eq} = C_1 A_2 + D_1 C_2$$

$$D_{eq} = C_1 B_2 + D_1 D_2$$



$$\overline{V}_s = A_{eq} \overline{V}_r + B_{eq} \overline{I}_r$$

$$\overline{I}_s = C_{eq} \overline{V}_r + D_{eq} \overline{I}_r$$

ph

DETERMINE THE EQUIVALENT A, B, C, D CONSTANTS OF THE GIVEN NETWORK.
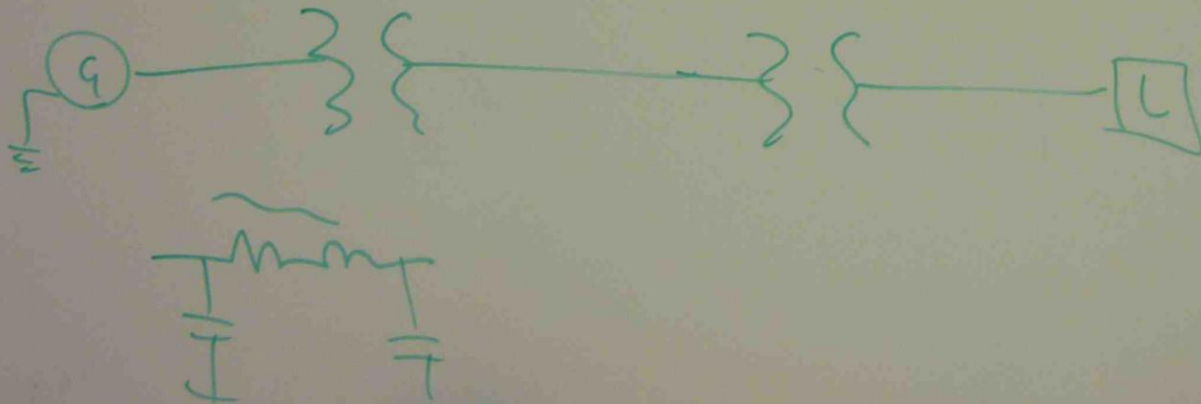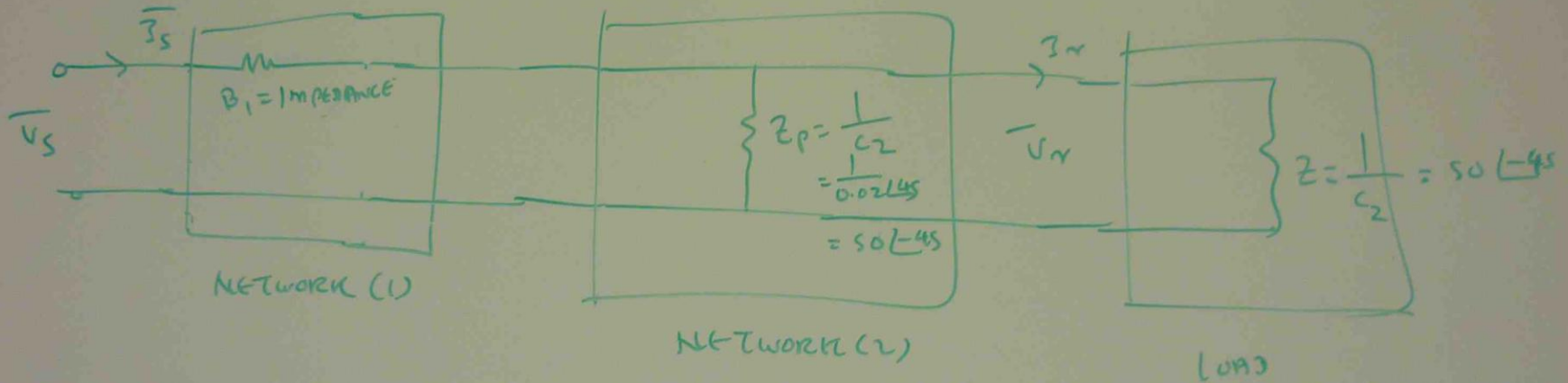
$$\begin{array}{llll} A_1 = 1.0 & B_1 = 20 \angle 30^\circ \Omega & C_1 = 0.05 & D_1 = 1.0 \\ A_2 = 1.0 & B_2 = 0 & C_2 = 0.02 \angle 45^\circ \text{ S} & D_2 = 1.0 \end{array}$$



$$A_{eg} = A_1 A_2 + B_1 C_2 = 1.0 \times 1.0 + 20 \angle 30^\circ \times 0.02 \angle 45^\circ$$

$$= 1 + 0.4 \angle 75^\circ$$

$$= 1 + 0.4 (\cos 75^\circ + j \sin 75^\circ)$$

$$= 1 + 0.4 (0.2598 + j 0.9659)$$

$$= 1 + 0.1 + j 0.4965$$

$$= 1.1 + j 0.4965$$

$$= \sqrt{1.1^2 + 0.4965^2} \angle \tan^{-1} \frac{0.4965}{1.1}$$

$$A_{eg} = 1.206 \angle 24.2^\circ$$

$$B_{eg} = A_1 B_2 + B_1 D_2 = 1.0 \times 0 + 20 \angle 30^\circ \times 1.0$$

$$= 0 + 20 \angle 30^\circ = 20 \angle 30^\circ$$

$$C_{eg} = C_1 A_2 + D_1 C_2 = 0 \times 1.0 + 1.0 \times 0.02 \angle 45^\circ$$

$$= 0.02 \angle 45^\circ$$

$$D_{eg} = C_1 B_2 + D_1 D_2$$

$$= 0 \times 0 + 1.0 \times 1.0$$

$$= 1.0$$

$$\bar{V}_S = A_{eg} \bar{V}_r + B_{eg} \bar{I}_r$$


$$= 1.206 \angle 24.2^\circ \bar{V}_r + 20 \angle 30^\circ \bar{I}_r$$

$$\bar{I}_S = C_{eg} \bar{V}_r + D_{eg} \bar{I}_r$$

$$= 0.02 \angle 45^\circ \bar{V}_r + 1.0 \bar{I}_r$$




OPEN CIRCUIT

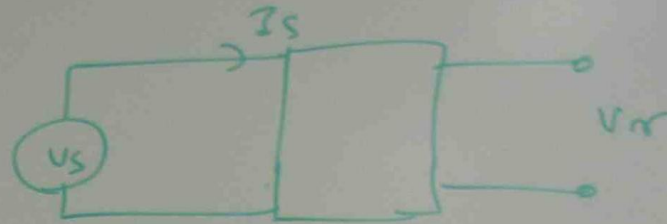

$$A_{eq} = \frac{V_s}{V_r}$$

$$C_{eq} = \frac{I_s}{V_s}$$

SHORT CIRCUIT

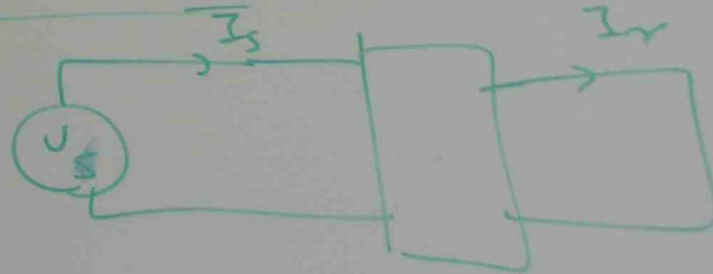

$$B_{eq} = \frac{V_s}{I_r}$$

$$D_{eq} = \frac{I_s}{I_r}$$

ph

DETERMINE THE A, B, C, D CONSTANTS OF THE NETWORK IN WHICH THE FOLLOWING TEST RESULTS HAVE BEEN OBSERVED.

RECEIVER OPEN CIRCUIT

$$\bar{V}_S = 100 \angle 0^\circ \text{ V}$$

$$\bar{V}_R = 70.7 \angle -45^\circ \text{ V}$$

$$\bar{I}_S = 1.41 \angle -45^\circ \text{ A}$$

$$\bar{I}_R = 0$$

RECEIVER SHORT CIRCUIT

$$\bar{V}_R = 0$$

$$\bar{V}_S = 100 \angle 0^\circ \text{ V}$$

$$\bar{I}_S = 2.0 \angle -90^\circ \text{ A}$$

$$\bar{I}_R = 2.0 \angle -90^\circ \text{ A}$$

SHORT

$$B = \frac{V_S}{I_R}$$

$$= \frac{100 \angle 0^\circ}{2.0 \angle 90^\circ}$$

$$= 50 \angle 90^\circ$$

$$D = \frac{I_S}{I_R} = \frac{2 \angle -90^\circ}{2 \angle -90^\circ}$$

$$= 1$$

OPEN

$$A = \frac{V_S}{V_R} = \frac{100 \angle 0^\circ}{70.7 \angle -45^\circ} = 1.41 \angle 45^\circ$$

$$C = \frac{I_S}{V_S} = \frac{1.41 \angle -45^\circ}{100 \angle 0^\circ} = 0.0141 \angle -45^\circ$$

D CONSTANTS OF THE NETWORK IN WHICH  
HAVE BEEN OBSERVED.

RECEIVER SHORT CIRCUIT

$$\bar{V}_r = 0$$

$$\bar{V}_s = 100 \angle 0^\circ \text{ V}$$

$$\bar{I}_s = 2.0 \angle -90^\circ \text{ A}$$

$$\bar{I}_r = 2.0 \angle -90^\circ \text{ A}$$

$$\frac{\angle 0}{\angle -45} = 1.41 \angle 45$$

$$\frac{41 \angle -45}{0 \angle 0} = 0.0141 \angle -45$$

SHORT

$$B = \frac{V_s}{I_r}$$

$$= \frac{100 \angle 0}{2.0 \angle 90}$$

$$= 50 \angle 90$$

$$D = \frac{I_s}{I_r} = \frac{2 \angle -90}{2 \angle -90}$$

$$= 1$$

$$\bar{V}_s = A \bar{V}_r + B \bar{I}_r$$

$$\bar{V}_s = 1.41 \angle 45 \bar{V}_r + 50 \angle 90 \bar{I}_r$$

$$\bar{I}_s = C \bar{V}_r + D \bar{I}_r$$

$$\bar{I}_s = 0.0141 \angle -45 \bar{V}_r + 1 \bar{I}_r$$