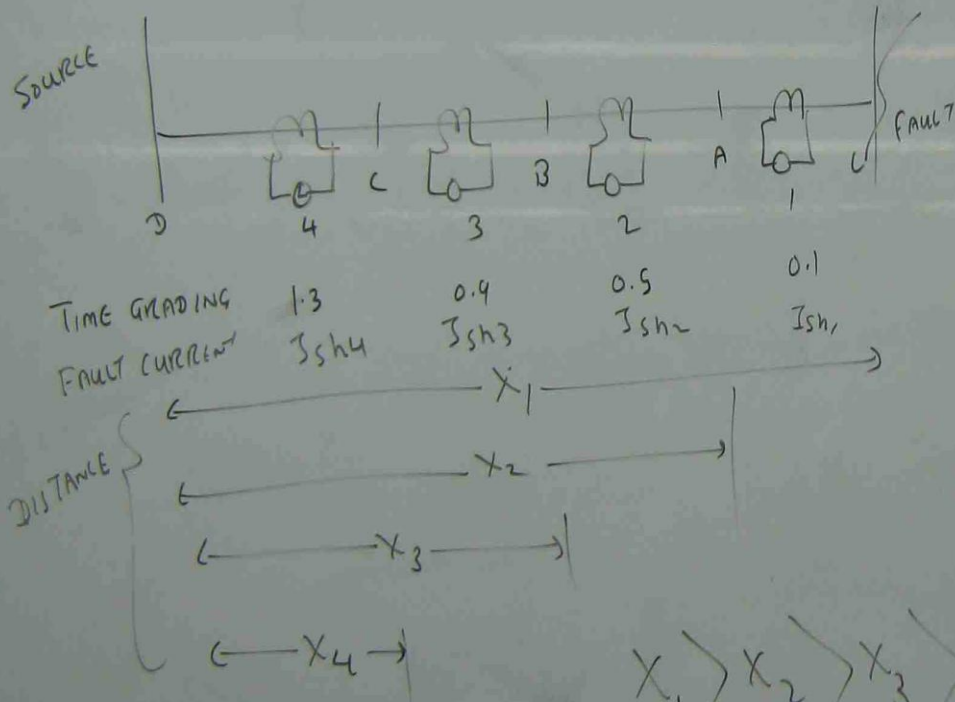


# TIME GRADING & CURRENT GRADING




$$X_1 > X_2 > X_3 > X_4$$

$$I_{sh1} < I_{sh2} < I_{sh3} < I_{sh4}$$

CURRENT GRADING.

10A 20A 30A 40A

① DRAW THE NORMAL POWER FLOW DIAGRAM

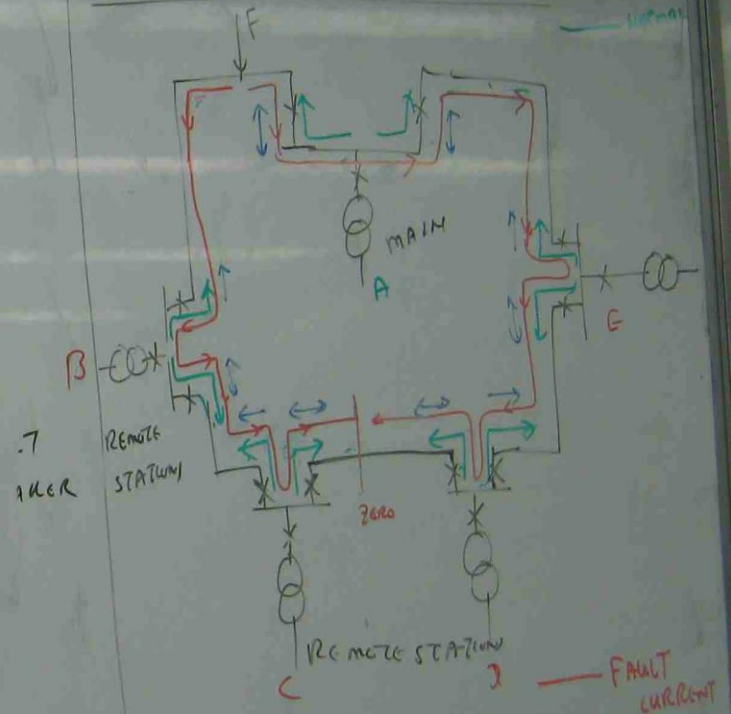

② DRAW THE FAULT CURRENT DIRECTION